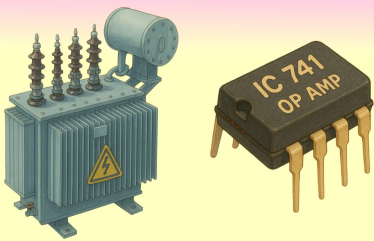


F. E. E. E.

Fundamentals of Electrical & Electronics Engineering Suggestion (2024-2025)

For 2nd Semester of Polytechnic

Top 150 Questions with Complete Answer From All Chapters



Prepared by NatiTute YouTube Channel

Contents

Sl No	Chapters	No. of Question	PDF Page No.
1	Overview of Electrical Components	21	3 to 5
2	Electric and Magnetic Circuits	24	6 to 9
3	A. C. Circuits	30	10 to 13
4	Transformer and Machines	23	14 to 17
5	Overview of Basic Semiconductor Devices	19	18 to 20
6	Overview of Analog Circuits	14	21 to 23
7	Overview of Digital Electronics	19	24 to 26
Total Number of Question=		150	

© Copyright Disclaimer

Any physical or digital format of this PDF are not allowed to share or re-selling without proper permission from NatiTute YouTube Channel.

এটা একটা পেইড pdf ebook যারা বইটি সংগ্রহ করবেন তাদের কাছে অনুমোদিত।
তোমরা এটা পেয়ার করে না, কারণ সবাইর কাছে pdf ফাইলটা পৌঁছে গেলে তোমরা
তাদের থেকে এগিয়ে থাকতে পারবে না এবং এই বই কলার কোনো মর্যাদা থাকবে না।

- Overview of Electrical Components ● FEEE Suggestion ● 2nd Semester ● WB Polytechnic
- 1. An ideal current source has-**
(a) zero internal resistance
(b) infinite internal resistance
(c) low value of voltage
(d) large value of current.
Explanation: An ideal current source is designed to supply a constant current regardless of the voltage across its terminals. To achieve this, it has infinite internal resistance, which ensures that the current remains constant even if the load resistance changes.
Answer: (b)
 - 2. The resistance of a conductor increases if its-**
(a) length increases
(b) area of cross-section increases
(c) length as well as area of cross-section increases
(d) value of specific resistance is kept constant.
Explanation: Resistance of a conductor:
$$R = \rho \frac{L}{A}$$

From this formula, it's clear that resistance (R) increases if the length (L) increases and decreases if the cross-sectional area increases.
Answer: (a)
 - 3. Rectifier is used to convert-**
(a) DC signal to AC signal
(b) AC signal to Pulsating DC signal
(c) Reducing the amplitude of DC signal
(d) Generation of AC signal
Explanation: A rectifier is an electrical device that converts an alternating current (AC) signal into a pulsating direct current (DC) signal by allowing current to flow in only one direction. This is commonly done using diodes in circuits like half-wave and full-wave rectifiers.
Answer: (b)
 - 4. For a DC voltage, an inductor-**
(a) is virtually a short circuit.
(b) is an open circuit.
(c) depends on polarity.
(d) depends on voltage value.
Explanation: An inductor opposes changes in current due to its property of self-inductance, but for a steady DC voltage, the current remains constant. This means the inductor behaves like a short circuit.
$$2U = \frac{1}{2} L (I_{max})^2$$

$$\Rightarrow 2I^2 = I_{max}^2$$

$$\Rightarrow I_{max} = \sqrt{2}I = 1.41I = 141.4\%$$

$$\therefore \% \text{ increased by } (141.4 - 100) = 41.4\%$$

Answer: (a)
 - 5. Define periodic and non-periodic waveforms with one example of each.**
Answer:
Periodic waveform: A waveform that repeats itself at regular intervals of time is called a periodic waveform.
Example: Sine wave, square wave, etc.
Non-periodic waveform: A waveform that does not repeat at regular time intervals is called a non-periodic (or aperiodic) waveform.
Example: A single pulse or a random noise signal.
 - 6. Energy is stored by the capacitor in the form of**
Explanation: A capacitor stores energy in the form of an electric field between its plates, known as electrostatic energy.
Answer: electrostatic energy.
 - 7. If two capacitance of $10 \mu F$ & $15 \mu F$ are connected in parallel then the equivalent capacitance will be**
Explanation: When capacitors are connected in parallel, their total or equivalent capacitance is the sum of the individual capacitances
$$= 10 \mu F + 15 \mu F = 25 \mu F$$

Answer: 25
 - 8. Give two examples of insulating material.**
Answer: Insulating materials resist the flow of electric current, preventing electrical leakage. Two examples of insulating material: Rubber and Glass.
 - 9. What is the frequency of a D.C signal?**
Answer: A DC signal has a constant value and does not change over time, so its frequency is zero.
 - 10. Energy stored by a coil is doubled when its current is increased by percent.**
(a) 25 (b) 50.5 (c) 41.4 (d) 100.
Explanation: The energy stored in a coil (inductor) is given by the formula: $U = \frac{1}{2} L I^2$
If the energy is doubled, we can write:
$$2U = \frac{1}{2} L (I_{max})^2$$

$$\Rightarrow 2I^2 = I_{max}^2$$



$$\Rightarrow I_{max} = \sqrt{2}I = 1.41I = 141.4\%$$

$$\therefore \% \text{ increased by } (141.4 - 100) = 41.4\%$$

Answer: (c)

● Overview of Electrical Components ● FEEE Suggestion ● 2nd Semester ● WB Polytechnic


- 11. Write the unit of resistivity.**
Answer: The unit of resistivity (ρ) in the International System of Units (SI) is ohm meter ($\Omega \cdot m$).
- 12. What is the unit of inductance?**
Answer: Unit of inductance is Henry (H). 1 Henry (H) is the inductance that induces 1 volt when current changes at 1 ampere per second.
- 13. What are the types of Rectifier available?**
Answer: Types of Rectifiers are Half-Wave Rectifier and Full-Wave Rectifier. Rectifiers convert AC into DC.
- 14. Name the factors affecting the resistance of a conductor.**
Answer: The resistance (R) of a conductor is affected by the following factors:
1) **Length of the Conductor (L):** Resistance is directly proportional to the length of the conductor. $R \propto L$
2) **Cross-Sectional Area (A):** Resistance is inversely proportional to the cross-sectional area of the conductor. $R \propto \frac{1}{A}$
3) **Resistivity of the Material (ρ):** Resistance depends on the nature of the material, represented by its resistivity. $R \propto \rho$
4) **Temperature:** For most conductors, resistance increases with an increase in temperature due to increased collisions between electrons and atoms. However, for some materials like semiconductors, resistance may decrease with temperature.
- 15. What do you mean by capacitance of a capacitor? What is its unit?**
Answer: The capacitance of a capacitor is the ability of the capacitor to store electric charge per unit voltage. It is defined as the ratio of the charge Q stored on the plates of the capacitor to the voltage V applied across the plates: $C = \frac{Q}{V}$
The SI unit of capacitance is the farad (F).
$$1 F = 1 \frac{C}{V}$$

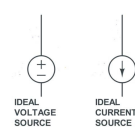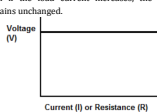Since a farad is a very large unit, practical capacitors are often measured in Microfarad (μF)
$$1 \mu F = 10^{-6} F$$
- 16. Define ideal current source and ideal voltage source with proper symbol.**
Answer:
Ideal Current Source: An ideal current source is a two-terminal element that delivers a constant current regardless of the voltage across it or the load connected to it. The output current remains unchanged even if the resistance or impedance of the connected circuit varies.
Ideal Voltage Source: An ideal voltage source is a two-terminal element that maintains a fixed voltage across its terminals, regardless of the current drawn by the connected circuit. The voltage remains constant even if the load resistance or impedance changes.

- 17. Draw the load current vs Load voltage curve of an ideal voltage source.**
Answer:
Ideal Voltage Source: An ideal voltage source maintains a constant voltage across its terminals regardless of the current drawn by the load. This means that even if the load current increases, the voltage remains unchanged.


[Prepared by NatiTute YouTube Channel]


● Overview of Electrical Components ● FEEE Suggestion ● 2nd Semester ● WB Polytechnic

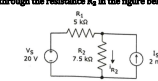- 18. How can you convert a voltage source into current source and vice-versa?**
Answer:
Converting a Voltage Source into a Current Source: A voltage source with a series resistance can be converted into an equivalent current source with a parallel resistance.
Conversion formula: $I_s = \frac{V_s}{R_s}$
Converting a Current Source into a Voltage Source: A current source with a parallel resistance can be converted into an equivalent voltage source with a series resistance.
Conversion formula: $V_s = I_s R_s$

- 19. What are active and passive components? Give examples for each.**
Answer:
Active Components: Active components are electronic components that can amplify signals, generate power, or control current flow. They require an external power source to operate and can introduce gain into a circuit.
Examples of Active Components:
1) **Transistors** - used for amplification and switching.
2) **Operational Amplifiers (Op-Amps)** - used in signal processing.
3) **Diodes** (e.g., LED, Zener diode) - allow current to flow in one direction.
Passive Components: Passive components do not require an external power source to operate. They cannot amplify signals but can store, dissipate, or control energy.
Examples of Passive Components:
1) **Resistors** - limit current and control voltage in circuits.
2) **Capacitors** - store and release electrical energy.
3) **Inductors** - store energy in a magnetic field and oppose changes in current.
4) **Transformers** - transfer electrical energy between circuits using electromagnetic induction.
- 20. Using source transformation principle, find out the current through the resistance R_2 .**

Solution: Current at voltage source (V_s)
$$I_s = \frac{V_s}{R_s} = \frac{26V}{10k} = 2.6mA$$

Since both current sources are in parallel, the equivalent current source is the algebraic sum of the two: $I_{eq} = 4mA - 2mA = 2mA$
The equivalent parallel resistance can be calculated using the formula: $R = \frac{R_1 R_2}{R_1 + R_2}$
$$\Rightarrow R = \frac{5k \times 7.5k}{5k + 7.5k} = \frac{37.5k}{12.5} = 3k\Omega = 3000\Omega$$
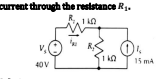
$$\therefore V = I_{eq} \times R = 2mA \times 3000\Omega = 6V$$

Finally, the current through R_2
$$I_{R_2} = \frac{V}{R_2} = \frac{6V}{7.5k\Omega} = 0.8mA \text{ (Ans)}$$
- 21. Using Source transformation principle find out the current through the resistance R_1 .**

Solution:
Given Circuit Details:
Voltage Source: $V_s = 40V$
Resistors: $R_1 = 1k\Omega$, $R_2 = 10k\Omega$
Current Source: $I_s = 15mA$
A voltage source V_s with a series resistance R_1 can be transformed into an equivalent current source:
$$I' = \frac{V_s}{R_1} = \frac{40V}{1k\Omega} = 40mA$$

Since both current sources are in parallel, we sum them up: $I_{eq} = 40mA + 15mA = 55mA$
The total parallel resistance is:
$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{1k \times 10k}{1k + 10k} = \frac{10k}{11} = 909\Omega$$

Now, the voltage across the parallel resistors:
$$V = I_{eq} \times R_{eq} = 55mA \times 909\Omega = \frac{55}{1000} \times 909 \times 1000 = 55 \times 909 = 50000V$$

$$\therefore \text{Current through } R_1:$$

$$I_{R_1} = \frac{V}{R_1} = \frac{50000V}{1000\Omega} = 50A = 27.5mA \text{ (Ans)}$$

[Prepared by NatiTute YouTube Channel]

● Electric and Magnetic Circuits ● FEEE Suggestion ● 2nd Semester ● WB Polytechnic

- 1. Which component opposes any change in current?**
(a) Resistor (b) Capacitor (c) Inductor (d) Diode
Explanation: An inductor opposes any change in current due to Lenz's Law. It stores energy in the form of a magnetic field and generates an induced electromotive force (EMF) that resists changes in current. This property is called inductive reactance.
Answer: (c)
- 2. The property of a material which opposes the creation of magnetic flux is called-**
(a) permeability (b) permittivity (c) reluctance (d) resistance.
Explanation: Reluctance is the property of a material that opposes the creation of magnetic flux in a magnetic circuit. It is analogous to resistance in an electrical circuit but applies to magnetism. The unit of reluctance is Ampere-turns per Weber (At/Wb).
Answer: (c)
- 3. The unit of magnetomotive force is-**
(a) ampere-turn (b) weber (c) mho (d) Maxwell.
Explanation: Magnetomotive force (MMF) is the force that drives magnetic flux through a magnetic circuit. It is measured in ampere-turns (At), which is the product of current (in amperes) and the number of turns in a coil.
Answer: (a)
- 4. A coil with 500 turns carries a current of 2 A. The value of MMF of the coil is (a) 20 AT (b) 200 AT (c) 1000 AT (d) 55 AT**
Explanation: The magnetomotive force (MMF) is calculated using the formula: $MMF = N \times I$
$$N = 500, I = 2A$$

$$\therefore MMF = 500 \times 2 = 1000 AT$$

Answer: (c)
- 5. The energy stored in a magnetic field is given by ($I =$ self inductance, $I =$ current)-**
(a) $\frac{1}{2} L I^2$ (b) $\frac{1}{2} L I$ (c) $I I^2$ (d) $I I^2$
Explanation: The energy (W) stored in the magnetic field of an inductor is given by the formula:
$$W = \frac{1}{2} L I^2$$

Where,
 L = Self-inductance (in Henry, H)
 I = Current (in Amperes, A)
Answer: (a)
- 6. Eddy current loss is directly proportional to**
(a) frequency f , maximum flux density, $(\phi)^2$ and $\frac{1}{R}$ (b) f and μ_m (c) f and μ_m (d) f^2 and μ_m
Explanation: Eddy current loss (P_e) in a magnetic material is given by the equation: $P_e \propto f^2 B_m^2$
Answer: (a)
- 7. The direction of induced emf is such that it will oppose the cause to which it is created, is related to**
(a) law of electromagnetic induction.
(b) Faraday's (c) Lenz's (d) Ohm's (e) Ampere's
Explanation: Lenz's Law states that: "The direction of the induced EMF (and hence the induced current) is always such that it opposes the change in magnetic flux that caused it."
Answer: (b)
- 8. Fleming's Left hand rule gives the direction of**
Explanation: Fleming's Left Hand Rule is used to find the direction of force acting on a current-carrying conductor in a magnetic field.
Answer: Force
- 9. Conductance in Electric circuit is analogous to _____ in Magnetic Circuit.**
Explanation: In an electric circuit, conductance (inverse of resistance) is analogous to reluctance in a magnetic circuit, which opposes magnetic flux.
Answer: reluctance
- 10. A motor converts electrical energy into _____ energy.**
Explanation: An electric motor converts electrical energy into mechanical energy, typically in the form of rotational motion.
Answer: mechanical
- 11. What do you mean by permeability?**
Answer:
Permeability (μ): Permeability is the property of a material that determines its ability to allow the formation of a magnetic field within it. It measures how easily a material can support the passage of magnetic flux when exposed to a magnetic field.
Mathematical Expression: $\mu = \frac{B}{H}$
Where:
 μ = Permeability (Henry per meter, H/m)
 B = Magnetic Flux Density (Tesla, T)
 H = Magnetizing Force (A/m)

11. Define the term Semiconductor.

Answer: A semiconductor is a material that has electrical conductivity between that of a conductor (like copper) and an insulator (like glass). Its conductivity can be controlled by temperature, impurities (doping), or an external electric field. Common semiconductors include silicon (Si) and germanium (Ge), which are widely used in electronic devices such as transistors, diodes, and integrated circuits.

12. Define the term Doping. Give examples of material for creation of p & n-type material.

Answer: Doping is the process of intentionally adding small amounts of impurities (called dopants) to a pure semiconductor (like silicon or germanium) to increase its conductivity by altering the number of charge carriers.

Types and Examples:


- n-type material** (adds electrons as majority carriers):
 - Formed by doping with pentavalent atoms (5 valence electrons)
 - Examples of dopants: Phosphorus (P), Arsenic (As), Antimony (Sb)
- p-type material** (adds holes as majority carriers):
 - Formed by doping with trivalent atoms (3 valence electrons)
 - Examples of dopants: Boron (B), Gallium (Ga), Indium (In)

13. Why is doping done on Semiconductor?

Answer: Doping is done on semiconductors to increase their conductivity by adding impurities. It creates n-type (electrons as majority carriers) or p-type (holes as majority carriers) semiconductors.

14. Draw the symbols of PNP and NPN transistor with proper notation.

Answer:

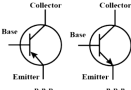

PNP: The arrow on the emitter points inward (indicating conventional current flow).

NPN: The arrow on the emitter points outward (indicating electron flow direction).

15. With respect to Energy band diagram differentiate between Conductors, Semiconductor & Insulator.

Answer:

Insulators:


- In case of insulators, the energy gap between the conduction and valence bands is very large and the conduction band is practically empty.
- When an electric field is applied to such kind of material, the conduction band remains to be empty. That is why no current flows through insulators.

Semiconductors:

- In case of semiconductor, the energy band structure is similar to insulator but in this case, the size of forbidden energy gap is quite smaller than that of the insulators.
- When an electric field is applied to a semiconductor, the electrons in the valence band find it relatively easier to jump to the conduction band. So, the conductivity of semiconductors lies between the conductivity of conductors and insulators.

Conductors:

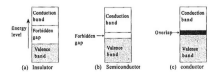- In the case of a conductor there is no forbidden gap, and the valence and conduction energy bands overlap. For this reason, very large numbers of electrons are available for conduction.
- Even when a small current is applied, conductors can conduct electricity.



16. Why is transistor termed as current controlled device?

Answer: A transistor is termed a current-controlled device because the output current (collector current, I_C) is controlled by the input current (base current, I_B).

In a Bipolar Junction Transistor (BJT):
 $I_C = \beta \cdot I_B$

Where:

I_C = collector current (output)

I_B = base current (input)

β = current gain of the transistor

This means a small base current controls a much larger collector current, hence it's called current-controlled. This property makes BJTs useful for amplification and switching.


17. Distinguish between an intrinsic and extrinsic semiconductor material.

Answer:

Intrinsic Semiconductor	Extrinsic Semiconductor
A pure semiconductor with no impurity atoms.	A semiconductor doped with impurity atoms to improve conductivity.
100% pure, only contains semiconductor atoms (e.g., Si, Ge).	Contains a small amount of impurity (dopant) added intentionally.
Equal number of electrons (n) and holes (p).	Carrier concentration is dominated by either electrons (n) or holes (p).
Low conductivity due to fewer charge carriers.	Higher conductivity due to increased free charge carriers from doping.
Fermi level lies near the center of the bandgap.	Fermi level shifts towards the conduction band in n-type and towards the valence band in p-type.
Conductivity increases with temperature.	Less affected by temperature due to dopant atoms.
Examples: Pure Silicon (Si), Pure Germanium (Ge).	Examples: Doped Silicon (Si) or Germanium (Ge) with P or As (n-type) or B or Al (p-type).

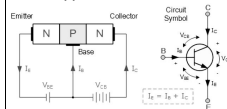18. Explain with diagram the principle of operation of an NPN transistor.

Answer: An NPN transistor consists of two n-type semiconductors separated by a p-type layer, forming the structure: Emitter (N) – Base (P) – Collector (N).




Working Principle:

- When the emitter-base junction is forward-biased, electrons (majority carriers in the N-type emitter) are injected into the base.
- The base is very thin and lightly doped, so only a few electrons recombine with holes.
- The majority of electrons pass through the base and reach the collector, which is reverse-biased and attracts them.

- A small base current I_B controls a large collector current I_C .
- This results in amplification, as the transistor transfers current from input to output.
 $I_C = \beta \cdot I_B$

19. Draw and explain the forward and reverse biased characteristics of P-N junction diode.

Answer:

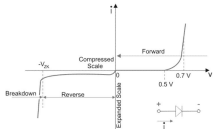

Forward Bias Characteristic:

- The depletion region narrows.
- The built-in potential barrier is reduced.
- Electrons from the N-side and holes from the P-side start moving toward the junction.
- At a certain voltage (threshold voltage), a large current starts flowing.
- Graph: The current exponentially increases after the threshold voltage is reached.

Reverse Bias Characteristic:

- The depletion region widens.
- The potential barrier increases.
- Only a very small leakage current flows due to minority carriers.
- At a high voltage (breakdown voltage), a large reverse current suddenly flows, leading to diode breakdown.
- Zener Breakdown: Occurs in heavily doped diodes at low voltage.
- Avalanche Breakdown: Occurs in lightly doped diodes at high voltage.
- Graph: A very small reverse current flows until breakdown, after which the current increases sharply.

(Prepared by [NafTute YouTube Channel](#))

1. An ideal OP-AMP is an ideal (a) current controlled current source (b) current controlled voltage source (c) voltage controlled voltage source (d) voltage controlled current source

Explanation: An ideal operational amplifier (OPAMP) is a voltage-controlled voltage source (VCVS) because it amplifies the difference between its two input voltages (the inverting and non-inverting inputs) to produce a much larger output voltage.
Answer: (c)

2. The expression of voltage gain in an inverting amplifier using ideal OP-AMP is (R_f = feedback resistance, R_i = input resistance)-

- $\frac{R_f}{R_i} \cdot \frac{V_{in}}{V_{out}}$
- $\frac{R_f}{R_i} \cdot \frac{V_{out}}{V_{in}}$
- $1 + \frac{R_f}{R_i}$
- $1 + \frac{R_i}{R_f}$

Explanation: For an ideal inverting amplifier using an op-amp, the voltage gain (A_v) is given by:
 $A_v = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$

The negative sign indicates a 180° phase shift between input and output.
Answer: (a)

3. The expression of voltage gain in a non-inverting amplifier using ideal OP-AMP is (R_f = feedback resistance, R_i = input resistance)-

- $\frac{R_f}{R_i} \cdot \frac{V_{in}}{V_{out}}$
- $\frac{R_f}{R_i} \cdot \frac{V_{out}}{V_{in}}$
- $1 + \frac{R_f}{R_i}$
- $1 + \frac{R_i}{R_f}$

Explanation: In a non-inverting amplifier using an ideal op-amp, the voltage gain is given by:
 $A_v = \frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_i}$

This configuration provides positive gain without phase inversion.
Answer: (c)

4. The CMRR of an Op-Amp is the ratio of ____.

Explanation: Common-Mode Rejection Ratio (CMRR) is the ratio of the differential gain to the common-mode gain, indicating how well the op-amp rejects common-mode signals.
Answer: Common-Mode Gain to Differential Mode Gain

5. An ideal OP-AMP has the following characteristics- (R_{in} = input resistance, A = open loop gain, R_{out} = output resistance)

- $R_{in} = \infty, A = \infty, R_{out} = 0$
 - $R_{in} = 0, A = \infty, R_{out} = 0$
 - $R_{in} = \infty, A = 0, R_{out} = \infty$
 - $R_{in} = 0, A = 0, R_{out} = \infty$
- Explanation:** An ideal operational amplifier (OP-AMP) has the following characteristics:
- Infinite input resistance ($R_{in} = \infty$):** This means no current flows into the input terminals of the OP-AMP.
 - Infinite open-loop gain ($A = \infty$):** The amplification of the input signal is infinite, meaning even a tiny difference between the inverting and non-inverting inputs would result in a huge output.
 - Zero output resistance ($R_{out} = 0$):** The OP-AMP can drive any load without any voltage drop across its output resistance.
- Answer:** (a)

6. Name the two input terminals of OP-AMP.

Answer: Two input terminals of an OP-AMP: Inverting (–) and Non-Inverting (+). These terminals receive input signals and determine the output behavior.

7. What is a dependent Source?

Answer: A dependent source is a voltage or current source whose value depends on another circuit variable.
Example: A current-controlled voltage source (CCVS) depends on an external current.


8. What is virtual ground?

Answer: **Virtual Ground:** Virtual ground is a concept used in op-amp circuits, particularly in inverting configurations, where the voltage at the inverting terminal is approximately 0V (ground) even though it is not physically connected to the ground. It helps in simplifying circuit analysis and ensures current flows correctly in feedback networks.

(Prepared by [NafTute YouTube Channel](#))

9. Draw the circuit diagram of an inverting amplifier and derive the expression for output voltage.

Answer:

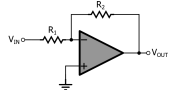

Derivation of Output Voltage Expression:

The non-inverting terminal (+) is grounded ($V_+ = 0$).
Due to virtual shorts concept, the inverting terminal (–) is also at 0V ($V_- = 0$).

Apply Kirchhoff's Current law at node V.
Since the input impedance of an ideal Op-Amp is infinite, no current enters the Op-Amp. So, the current through R_1 must be equal to the current through R_2 :


$$\begin{aligned} I_1 = I_2 \\ \Rightarrow \frac{V_{in} - 0}{R_1} = -\frac{V_{out} - 0}{R_2} \\ \Rightarrow \frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2} \\ \Rightarrow V_{out} = -V_{in} \times \frac{R_2}{R_1} \end{aligned}$$

The output is 180° out of phase with the input due to the negative sign.

The gain is given by $A_v = -\frac{R_2}{R_1}$.

10. Explain the op-amp acts as a adder circuit.

Answer:

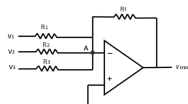

Working Principle of Op-Amp Adder:

The inverting terminal (–) is at virtual ground (due to the high gain of the Op-Amp). Since no current flows into the Op-Amp, all input currents sum up and pass through the feedback resistor R_f . By Kirchhoff's Current Law (KCL) at the inverting terminal:

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_{out}}{R_f} = 0$$


For equal resistors ($R_1 = R_2 = R_f = R$)

$$\Rightarrow V_{out} = -\frac{R}{R} (V_1 + V_2 + V_3)$$

The output is inverted (negative sign).

11. Draw the circuit diagram of a non inverting amplifier with feedback using op-amp & derive the expression of gain.

Answer:

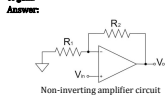

V_{in} = input voltage, V_{out} = out voltage
 R_1 = resistor connected to ground from inverting input
 R_2 = feedback resistor
Since the op-amp has very high gain, the voltage at the inverting terminal (V_-) is equal to the voltage at the non-inverting terminal (V_+). $V_- = V_+ = V_{in}$

The current through R_1 is the same as the current through R_2 because of Kirchhoff's Current Law. Applying Ohm's Law: The current through R_1 is:

$$I = \frac{V_- - V_{out}}{R_1 - R_2}$$


The same current flows through R_2 , so the voltage drop across R_2 is: $V_{out} - V_- = I \cdot R_2$
 $\Rightarrow V_{out} - V_{in} = \frac{V_{in} - V_{out}}{R_1} \cdot R_2$
 $\Rightarrow V_{out} = \frac{V_{in}}{R_1} \cdot R_2 + V_{in}$
 $\Rightarrow V_{out} = V_{in} \left(1 + \frac{R_2}{R_1} \right)$

$\therefore$ Voltage gain $A_v = \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$

(Prepared by [NafTute YouTube Channel](#))

12. Draw the pin diagram of IC 741 OPAMP.

Answer:

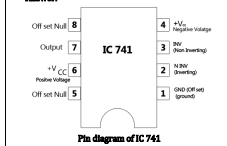

Pin Number	Pin Name
1	Offset Null
2	Inverting Input (–)
3	Non-Inverting Input (+)
4	Vcc (+) / GND
5	Offset Null
6	Output
7	Vcc (+)
8	NC (No Connection)

13. Describe the function of each pin of IC 741 OPAMP

Answer:

Pin No.	Function
1	Used for offset voltage adjustment (with Pin 5) to make output exactly zero when input is zero.
2	Input terminal where signal is applied with inverted phase (180° shift).
3	Input terminal where signal is applied with the same phase.
4	Connected to the negative power supply (e.g., –15V).
5	Used along with Pin 1 for zero offset voltage adjustment.
6	Provides the amplified output signal.
7	Connected to the positive power supply (e.g., +15V).
8	Not internally connected, usually unused.

(Prepared by [NafTute YouTube Channel](#))

1. When the two input of a NAND gate is high, the output of the gate will be (a) High (b) Low (c) Toggle between high & low (d) none of the above

Explanation: A NAND gate (NOT AND) gives a low output only when all its inputs are high. Its operation is the inverse of an AND gate.
Answer: (b)

2. Which of these sets of logic gates are known as universal gates? (a) XOR, NAND, OR (b) OR, NOT, XOR (c) NOR, NAND, XOR (d) NOR, NAND.

Explanation: NAND and NOR gates are called universal gates because by combining multiple NAND or NOR gates, you can create all basic logic functions like AND, OR, and NOT.
Answer: (d)

3. When two input of a NAND gate is high, the output of the gate will be (a) High (b) Low (c) Toggle between high & low (d) none of the above

Explanation: A NAND gate is essentially an AND gate followed by a NOT gate. An AND gate outputs high only when all inputs are high. The NOT gate inverts the output of the AND gate, so a high output from the AND gate becomes a low output from the NAND gate, and vice versa.
Answer: (b)

4. The number of flip-flops required in a decade counter is- a) 2 b) 3 c) 4 d) 10.

Explanation: The number of flip-flops required is determined by: $2^n \geq 10$, where n is the number of flip-flops.
 $2^3 = 8$ (not enough)
 $2^4 = 16$ (sufficient)
Thus, 4 flip-flops are needed to count from 0 to 9 in a decade counter.
Answer: (c)

5. The maximum possible number of states in a ripple counter with 5 flip-flops is- (a) 32 (b) 16 (c) 10 (d) 5.

Explanation: A ripple counter with n flip-flops can have a maximum of 2^n states.
For 5 flip-flops: $2^5 = 32$
Answer: (a)

6. $\bar{A} + B$ is equivalent to- (a) $A + B$ (b) $A \cdot B$ (c) $\bar{A} \cdot \bar{B}$ (d) $\bar{A} + \bar{B}$

Explanation: The given expression is $\bar{A} + B$. According to De Morgan's Law, the negation of the sum of two variables is equal to the product of their negations:
 $\overline{A + B} = \bar{A} \cdot \bar{B}$
Answer: (b)

7. The output of AND gate will be HIGH only when both the inputs is ____.

Explanation: In an AND gate, the output is HIGH (1) only when both inputs are HIGH (1). Otherwise, the output is LOW (0).
Answer: HIGH

8. The full form of TTL is ____.

Explanation: TTL is a type of logic family that uses transistors to perform logic operations, typically used in digital circuits.
Answer: Transistor-Transistor Logic

9. Define the term Flip-Flop?

Answer: A Flip-Flop is a bistable multivibrator, which is a digital electronic circuit used to store one bit of data. It has two stable states (logic 0 and logic 1) and can change states based on input signals. Flip-flops are the fundamental building blocks of sequential logic circuits and are commonly used in memory elements, registers, and counters.

10. Name any two types of Flip-Flop.

Answer: Two types of Flip-Flops: SR Flip-Flop and D Flip-Flop. Flip-flops store binary data and are used in memory and sequential circuits.

(Prepared by [NafTute YouTube Channel](#))

11. State De-Morgan's Theorem.

Answer:

De Morgan's Laws in Boolean Algebra: De Morgan's Theorem provides an equivalence between AND, OR, and NOT operations. They state:

First Law: The complement of a product is equal to the sum of the complements.

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

Proof:

A	B	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

Since $\overline{A \cdot B}$ and $\overline{A} + \overline{B}$ produce the same output, 1st Law is proved.

Second Law: The complement of a sum is equal to the product of the complements.

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

Proof:

A	B	$\overline{A + B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Since $\overline{A + B}$ and $\overline{A} \cdot \overline{B}$ produce the same output, 2nd Law is proved.

12. Draw the NOR gate and write down its truth table.

Answer:

NOR gate:



Boolean Expression: $Z = \overline{A + B}$

Truth Table for NOR Gate:

Input A	Input B	Output $Z = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

(Prepared by [NestTute](#) YouTube Channel)

13. Draw the logic symbol and truth table of a 2-input NAND gate and EX-OR gate.

Answer:

2-input NAND gate:




Logic Symbol: 2-input NAND gate

Boolean Expression: $Y = \overline{A \cdot B}$

Truth Table:

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

2-input EX-OR gate:

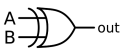

Logic Symbol: 2-input EX-OR gate

Boolean Expression: $Y = A \cdot \overline{B} + \overline{A} \cdot B = A \oplus B$

Truth Table of XOR Gate

A	B	Y = $A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

14. Draw the symbol of two input EX-NOR gate.

Answer:



Truth Table

Input A	Input B	Output
0	0	1
0	1	0
1	0	0
1	1	1

2-input EX-NOR gate

15. What are universal logic gates? Give examples.

Answer:

Universal Gates: Universal gates are logic gates that can be used to implement any Boolean function without needing other types of gates.

Examples: The NAND and NOR gates are called universal gates.

NAND and NOR Called Universal Gates because-

1. Functional Completeness: Any Boolean function can be designed using only NAND or NOR gates.

2. Replacement for Basic Gates: These gates can replicate the functions of AND, OR, and NOT gates.

3. Practicality in Circuit Design: Using only one type of gate (NAND or NOR) simplifies hardware design and reduces manufacturing costs.

16. Simplify the expression using Boolean algebra and realize the same by using logic gates.

$$Y = (A + B + C) \cdot (A + BC)$$

Answer:

$$Y = (A + B + C) \cdot (A + BC)$$

Using distributive:

$$Y = A(A + BC) + (B + C)(A + BC)$$

Using Absorption Law ($A + ABC = A$):

$$Y = A + (B + C)(A + BC)$$

Expanding ($(B + C)(A + BC)$):


$$Y = A + BA + BB C + CA + CBC$$

Using Idempotent Law ($BB = B$):

$$Y = A + BA + BC + CA + CBC$$

Using Absorption ($A + BA = A$):

$$Y = A + BC$$

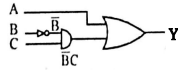


17. What is the minimum number of NAND gates required to realize a XOR gate.

Answer: An XOR (Exclusive-OR) gate gives a high output (1) only when the inputs are different.

The Boolean expression for XOR is:

$$A \oplus B = A'B + AB'$$

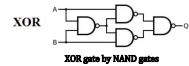This can be implemented using 4 NAND gates:



XOR gate by NAND gates

18. Give two applications of flip-flop.

Answer: Two applications of flip-flop are-

- 1) **Data Storage (1-bit Memory Cell):** Flip-flops are used to store a single bit of data (0 or 1). In digital systems, multiple flip-flops can be combined to create registers, which store multi-bit binary data in CPUs and memory systems.
- 2) **Counters and Timers:** Flip-flops are the building blocks of counters (e.g., ripple counters, synchronous counters) used in digital clocks, frequency dividers, and timers. They help in counting events or generating precise time delays.

19. What is decade counter?

Answer: A decade counter is a digital counter that counts from 0 to 9 (ten states) and then resets to 0 on the next clock pulse. It typically uses 4 flip-flops and is designed to output a binary sequence representing decimal digits. After reaching the binary equivalent of 9 (1001), it resets to 0000, making it useful for applications like digital clocks, frequency division, and event counting. Decade counters can be either synchronous or asynchronous depending on how the flip-flops are triggered.

(Prepared by [NestTute](#) YouTube Channel)